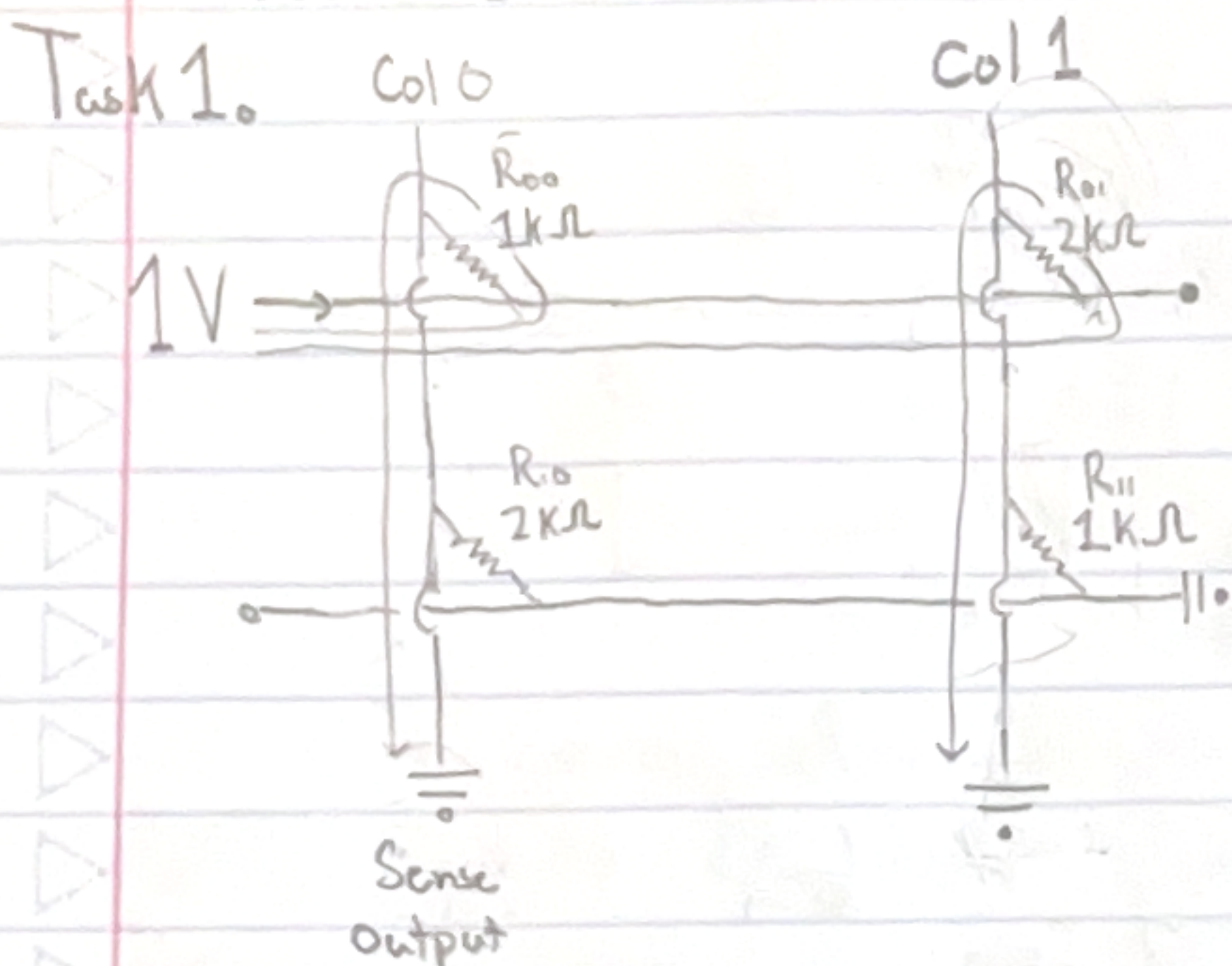


CodeTest 6. CMAN



$$E_{\text{ffective resistance}} = 1 / \left(\frac{1}{1k\Omega} + \frac{1}{2k\Omega} \right)$$


$$E_{\text{ffective resistance}} = 666\Omega$$

$$\text{Total flow} = 1.5\text{mA}$$

Since resistance ratio is 1 to 2,

$2/3$ flows through R_{00} and $1/3$ flows

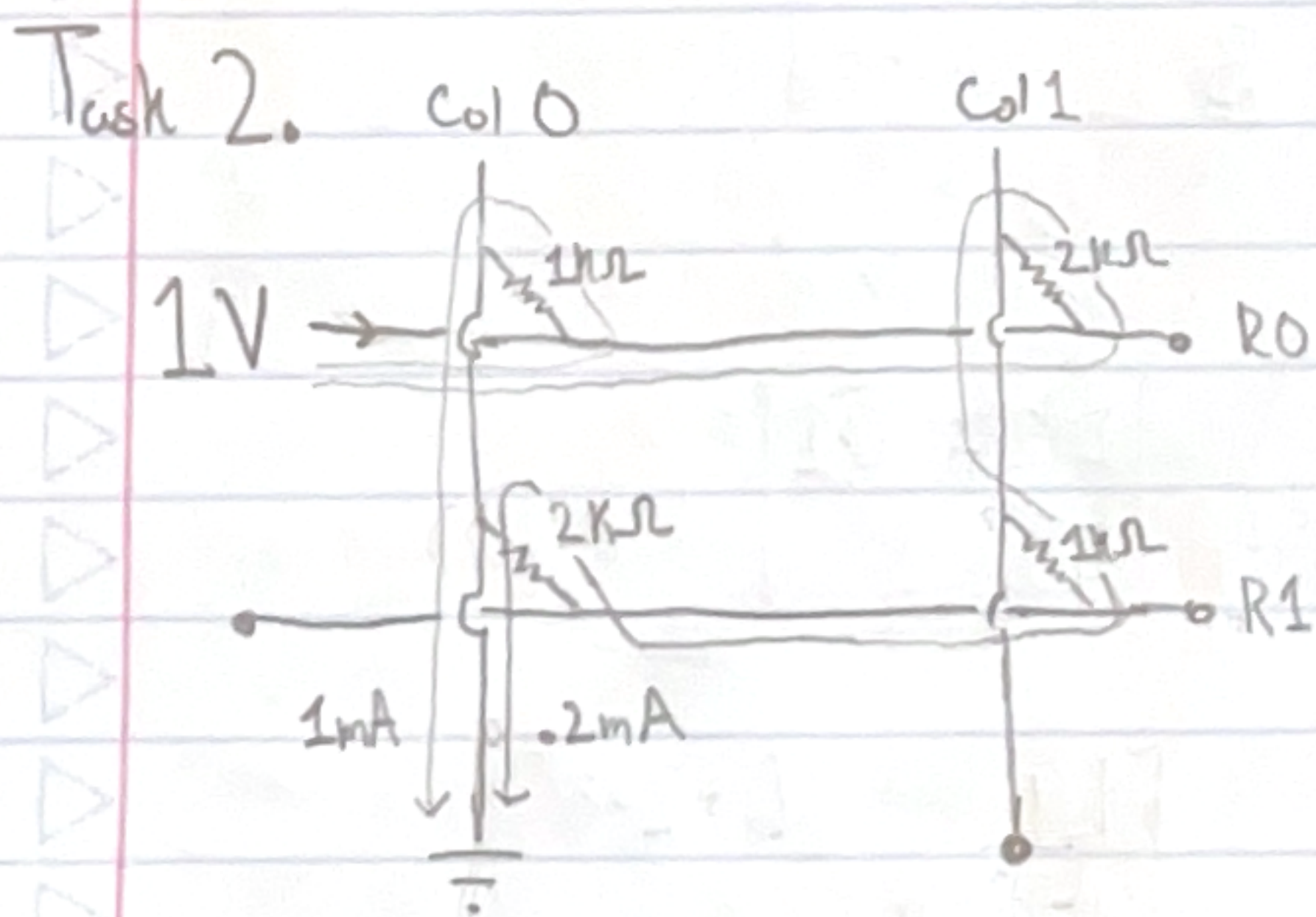through R_{01} . $I_0 = 1\text{mA}$, $I_1 = .5\text{mA}$.



$$E_{\text{ffective resistance}} = 1 / \left(\frac{1}{1k\Omega} + \frac{1}{2k\Omega + 1k\Omega + 2k\Omega} \right) = 833\Omega$$

$$\text{Total flow} = 1V / 833\Omega = 1.2\text{mA}$$

with sneak current, 20% more

flow. Sneak path flow is .2mA, so

$$V(\text{col1}) = 1V - 2k\Omega \cdot .2\text{mA} = 1V - .4V = .6V \text{ and}$$

$$V(\text{row1}) = .6V - 1k\Omega \cdot .2\text{mA} = .6V - .2V = .4V.$$

Task 3. The sneak path provides an additional undesired component to the dot product. This is an issue for large matrices, as the larger the matrix, the more sneak paths will become available. This will result in larger and larger perturbations to the correct output as matrix size increases.